

UNIVERSITY OF BOLTON
SCHOOL OF ENGINEERING
BSc(Hons) MECHATRONICS
SEMESTER ONE EXAMINATION 2021-22
ELECTRONIC ENGINEERING FOR MECHATRONICS
MODULE NO: MEC6005

Date: Thursday 13th January 2022

Time: 14:00 – 16:00

INSTRUCTIONS TO CANDIDATES:

There are **SIX** questions.

Answer any **FOUR** questions.

All questions carry equal marks.

Marks for parts of questions are shown in brackets.

This examination paper carries a total of 100 marks.

Formulae sheet is attached at the end of the paper.

All working must be shown. A numerical solution to a question obtained by programming an electronic calculator will not be accepted.

Question 1

a) Define the following terms (1.5 marks for each definition):

- i. Frequency
- ii. Period
- iii. Phase angle
- iv. Peak to peak value
- v. RMS value
- vi. Internal resistance
- vii. Current
- viii. Resistance

[12 marks]

b) An AC ammeter reads 11A rms current through a resistive load, and a voltmeter reads 360V rms drop across the load.

(i) What are the peak values and the average values of the alternating current and voltage? [6 marks]

(ii) Calculate the load resistance. [2 marks]

c) Find the Thevenin equivalent of the circuit given in Figure Q1 below. [5 marks]

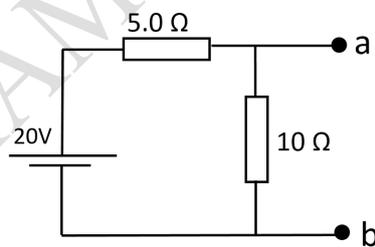


Fig.Q1

Total: 25 marks

PLEASE TURN THE PAGE....

Question 2

- a) For the circuit shown below (Figure Q2a), considering the R_{Load} as the load resistance

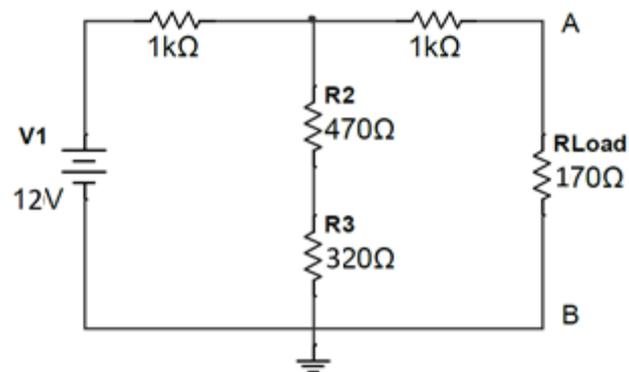


Figure Q2a

- (i) Derive the equivalent Thevenin circuit between points "A" and "B" **[10 marks]**
- (ii) Derive the equivalent Norton circuit between points "A" and "B" **[5 marks]**
- b) For the following circuit (Figure Q2b), using superposition theorem or otherwise, find out the current flowing through the $10\ \Omega$ resistor.

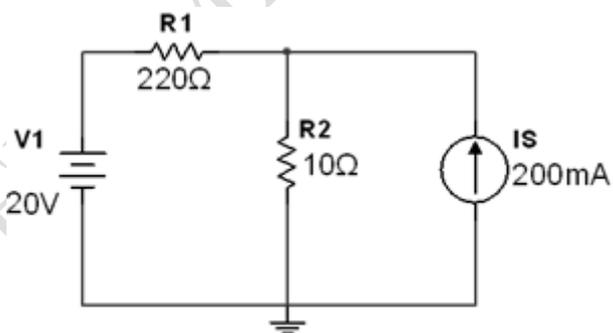


Figure Q2b

[10 marks]

Total: 25 marks

PLEASE TURN THE PAGE....

Question 3

- a) A $13\ \mu\text{F}$ capacitor has $12\ \text{V}$ across it. What quantity of charge is stored in it? **[5 marks]**

- b) Draw a diagram of a parallel plate capacitor showing the charge on the plates and the E field in the region between the plates. **[5 marks]**
- c) Explain what is meant by the dielectric strength E_m of an insulator? **[5 marks]**
- d) For the capacitor **charging** circuit shown in Figure Q3d below, where the capacitor is initially discharged, sketch two separate graphs for the current I versus time and the capacitor voltage V_c versus time. **[5 marks]**

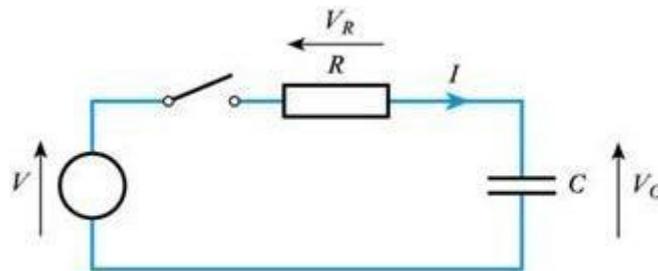


Figure Q3d - An initially uncharged capacitor being charged through a resistor.

- e) Explain with the assistance of a diagram what happens to the structure of the curves for I versus time and V_c versus time if the time constant $\tau = RC$ for the circuit increases? **[5 marks]**

Total: 25 marks

PLEASE TURN THE PAGE....

Question 4

For the circuit shown in figure Q4, calculate:

- a) Currents I_1 , I_2 , and I_3 **[9 marks]**
- b) Voltages across R_1 , R_2 , and R_3 **[6 marks]**

- c) Powers P1, P2, and P3 [3 marks]
- d) Draw the complete voltages and currents phasor diagram [3 marks]
- e) The peak I3 current at resonance frequency [4 marks]

Where $v = 17\cos 314t$, $R_1 = R_2 = 2\Omega$, $R_3 = 4\Omega$, $X_{L2} = j2\Omega$, $X_{L3} = j6\Omega$, $X_C = -j4\Omega$

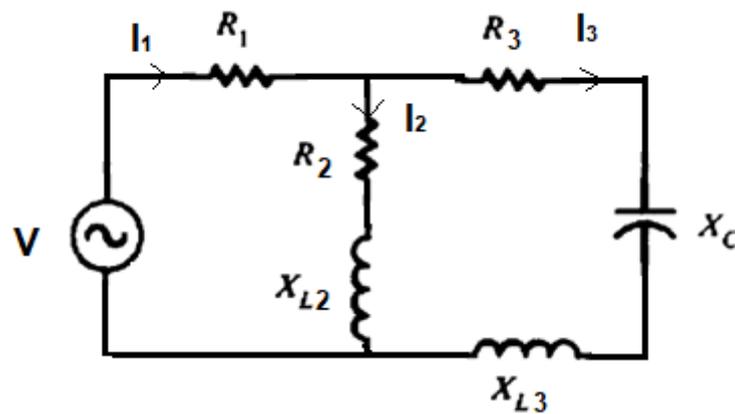


Figure Q4

Total: 25 marks

PLEASE TURN THE PAGE....

Question 5

- (i) the value of unknown resistance between point A & B and [7 marks]
(ii) the total current supplied by the battery. [7 marks]

b) Use network conversion to find the total current of the circuit in figure 6b

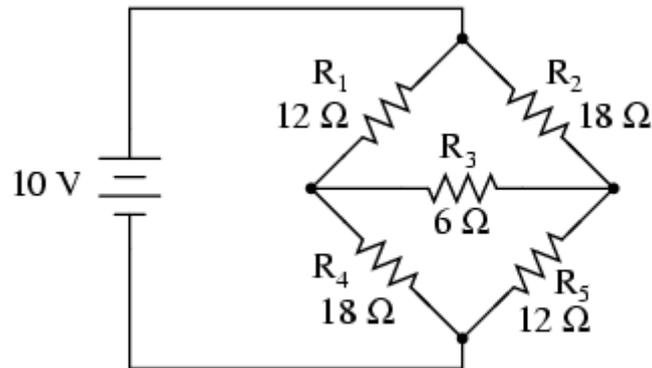


Figure 6b

[11 marks]

Total: 25 marks

END OF QUESTIONS

Formula sheet follows on next page....

PLEASE TURN THE PAGE....

APPENDIX: Formula Sheet

The following symbols in the formulae have their standard meaning:

Ohm's law: $V = IR$

Power: $P = IV$

Magnetic flux: $\Phi = BA$

Induced voltage: $V = \Delta\Phi/\Delta t$

Force experienced by charged particle = $qvB\sin\theta$

Motional emf: $E = Blv$ $f = \frac{pn}{120}$

Magnitude of the Reactance of Inductor L : $X_L = 2\pi fL$

Magnitude of the Reactance of Capacitor C : $X_C = \frac{1}{2\pi fC}$

Pythagorean theorem: $c^2 = a^2 + b^2$

Tangent function: $\tan A = \text{opposite/adjacent}$

$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$, $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$

$H = \frac{NI}{l}$, $B = \mu H$

MMF = $N \cdot I$

$L = \frac{\mu_0 \mu_r AN^2}{l}$, $E = \frac{1}{2} LI^2$


$C = Q/V$, $C = \frac{\epsilon A}{d}$, $E = \frac{1}{2} CV^2$

$v_L = L \cdot \frac{di_L}{dt}$

$i_C = C \frac{dv_C}{dt}$

$f = \frac{pn}{120}$

⊕ Three-phase systems:

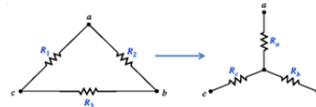


Delta to Star conversion:

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$
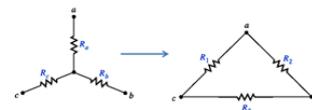
$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$



Star to Delta conversion:

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

PLEASE TURN THE PAGE....

Multiply the Value	By	To Get the Value
Peak	2	Peak-to-peak
Peak-to-peak	0.5	Peak
Peak	0.637	Average
Average	1.570	Peak
Peak	0.707	RMS (effective)
RMS (effective)	1.414	Peak
Average	1.110	RMS (effective)
RMS (effective)	0.901	Average

Summary Table for Series and Parallel RL Circuits

X_L and R in Series	X_L and R in Parallel
<p>I the same in X_L and R</p> <p>$V_T = \sqrt{V_R^2 + V_L^2}$</p> <p>$Z = \sqrt{R^2 + X_L^2} = \frac{V_T}{I}$</p> <p>$V_R$ lags V_L by 90°</p> <p>$\theta = \arctan \frac{X_L}{R}$</p>	<p>V_T the same across X_L and R</p> <p>$I_T = \sqrt{I_R^2 + I_L^2}$</p> <p>$Z_T = \frac{V_T}{I_T}$</p> <p>$I_L$ lags I_R by 90°</p> <p>$\theta = \arctan \left(-\frac{I_L}{I_R} \right)$</p>

Summary Table for Series and Parallel RC Circuits

X_C and R in Series	X_C and R in Parallel
<p>I the same in X_C and R</p> <p>$V_T = \sqrt{V_R^2 + V_C^2}$</p> <p>$Z = \sqrt{R^2 + X_C^2} = \frac{V_T}{I}$</p> <p>$V_C$ lags V_R by 90°</p> <p>$\theta = \arctan \left(-\frac{X_C}{R} \right)$</p>	<p>V_T the same across X_C and R</p> <p>$I_T = \sqrt{I_R^2 + I_C^2}$</p> <p>$Z_T = \frac{V_T}{I_T}$</p> <p>$I_C$ leads I_R by 90°</p> <p>$\theta = \arctan \frac{I_C}{I_R}$</p>

END OF PAPER